

JEE Mains 2019 Chapter wise Question Bank

Alternating Current - Questions


Q1

A series AC circuit containing an inductor (20 mH), a capacitor (120 μ F) and a resistor (60 Ω) is driven by an AC source of 24 V/50 Hz. The energy dissipated in the circuit in 60 s is:

- (1) 5.65×10^2 J (2) 2.26×10^3 J
(3) 5.17×10^2 J (4) 3.39×10^3 J

9 Jan Evening

Q2

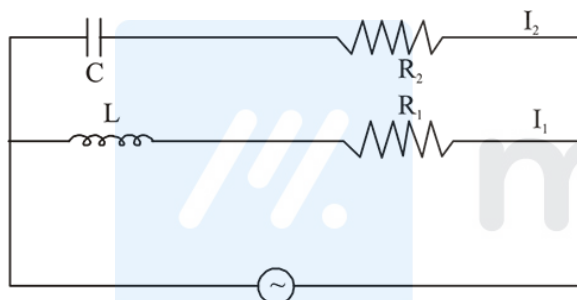

In the above circuit, $C = \frac{\sqrt{3}}{2} \mu\text{F}$, $R_2 = 20 \Omega$, $L = \frac{\sqrt{3}}{10} \text{ H}$ and

$R_1 = 10 \Omega$. Current in L- R_1 path is I_1 and in C- R_2 path it is I_2 .

The voltage of A.C source is given by, $V = 200\sqrt{2} \sin(100t)$ volts. The phase difference between I_1 and I_2 is :

- (1) 60° (2) 30°
(3) 90° (4) 0

12 Jan Evening

Q3

An alternating voltage $v(t) = 220 \sin 100\pi t$ volt is applied to a purely resistive load of 50Ω . The time taken for the current to rise from half of the peak value to the peak value is :

- (1) 5 ms (2) 2.2 ms (3) 7.2 ms (4) 3.3 ms

8 April Morning

Q4

A circuit connected to an ac source of $emf e = e_0 \sin(100t)$ with t in seconds, gives a phase difference of $\frac{\pi}{4}$ between the $emf e$ and current i . Which of the following circuits will exhibit this ?

- (1) RL circuit with $R = 1 \text{ k}\Omega$ and $L = 10 \text{ mH}$
(2) RL circuit with $R = 1 \text{ k}\Omega$ and $L = 1 \text{ mH}$
(3) RC circuit with $R = 1 \text{ k}\Omega$ and $C = 1 \mu\text{F}$
(4) RC circuit with $R = 1 \text{ k}\Omega$ and $C = 10 \mu\text{F}$.

8 April Evening

JEE Mains 2019 Chapter wise Question Bank

Alternating Current - Answers


Q1

- (3) Given: $R = 60\Omega$, $f = 50 \text{ Hz}$, $\omega = 2\pi f = 100\pi$ and $v = 24\text{V}$
 $C = 120 \mu\text{f} = 120 \times 10^{-6}\text{f}$

$$x_C = \frac{1}{\omega C} = \frac{1}{100\pi \times 120 \times 10^{-6}} = 26.52\Omega$$

$$x_L = \omega L = 100\pi \times 20 \times 10^{-3} = 2\pi\Omega$$

$$x_C - x_L = 20.24 \approx 20$$

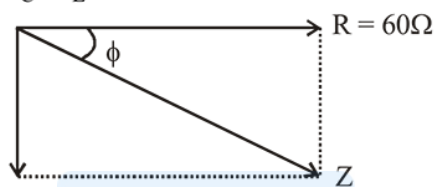

$$Z = \sqrt{R^2 + (x_C - x_L)^2}$$

$$Z = 20\sqrt{10}\Omega$$

$$\cos \phi = \frac{R}{Z} = \frac{60}{20\sqrt{10}} = \frac{3}{\sqrt{10}}$$

$$P_{\text{avg}} = VI \cos \phi, I = \frac{V}{Z} = \frac{V^2}{Z} \cos \phi = 8.64 \text{ watt}$$


Energy dissipated (Q) in time $t = 60\text{s}$ is

$$Q = Pt = 8.64 \times 60 = 5.17 \times 10^2 \text{J}$$

9 Jan Evening

Q2

(Bonus)

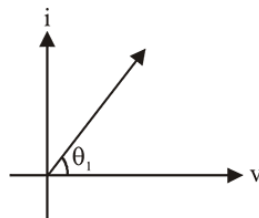

Capacitive reactance,


$$X_c = \frac{1}{\omega C} = \frac{4}{10^{-6} \times \sqrt{3} \times 100} = \frac{2 \times 10^4}{\sqrt{3}}$$

$$\tan \theta_1 = \frac{X_C}{R_2} = \frac{10^3}{\sqrt{3}}$$

θ_1 is close to 90°

For L-R circuit
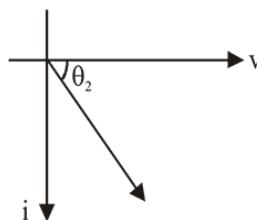
$$X_L = \omega L = 100 \times \frac{\sqrt{3}}{10} = 10\sqrt{3}$$



$$R_1 = 10$$

$$\tan \theta_2 = \frac{X_L}{R_1}$$

$$\tan \theta_2 = \sqrt{3} \Rightarrow \theta_2 = \tan^{-1}(\sqrt{3})$$

$$\theta_2 = 60^\circ$$

So, phase difference comes out $90^\circ + 60^\circ = 150^\circ$

If R_2 is $20 \text{ K}\Omega$

then phase difference comes out to be $60 + 30 = 90^\circ$.

Therefore Ans. is **Bonus**

12 Jan Evening

Q3

(4) As $V(t) = 220 \sin 100 \pi t$

$$\text{so, } I(t) = \frac{220}{50} \sin 100 \pi t$$

$$\text{i.e., } I = I_m = \sin(100 \pi t)$$

For $I = I_m$

$$t_1 = \frac{\pi}{2} \times \frac{1}{100\pi} = \frac{1}{200} \text{ sec.}$$

$$\text{and for } I = \frac{I_m}{2}$$

$$\Rightarrow \frac{I_m}{2} = I_m \sin(100 \pi t_2)$$

$$\Rightarrow \frac{\pi}{6} = 100 \pi t_2 \Rightarrow t_2 = \frac{1}{600} s$$

$$\therefore t_{\text{req}} = \frac{1}{200} - \frac{1}{600} = \frac{2}{600} = \frac{1}{300} s = 3.3 \text{ ms}$$

8 April Morning

Q4

(4) $\omega = 100 \text{ rad/s}$

We know that

$$\tan \phi = \frac{X_C}{R} = \frac{1}{\omega CR}$$

$$\text{or } \tan 45^\circ = \frac{1}{\omega CR}$$

$$\text{or } \omega CR = 1$$

$$\text{LHS: } \omega CR = 10 \times 10 \times 10^{-6} \times 10^3 = 1$$

8 April Evening