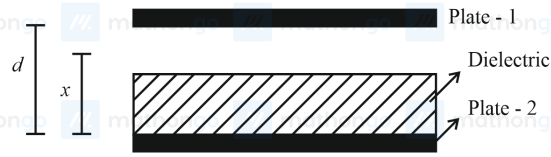



1. A parallel plate capacitor with plate area A and plate separation d is filled with a dielectric material of dielectric constant $K = 4$. The thickness of the dielectric material is x , where $x < d$.



Let C_1 and C_2 be the capacitance of the system for $x = \frac{1}{3}d$ and $x = \frac{2d}{3}$, respectively. If $C_1 = 2 \mu\text{F}$, the value of C_2 is _____ μF .

[2023 (06 Apr Shift 1)]

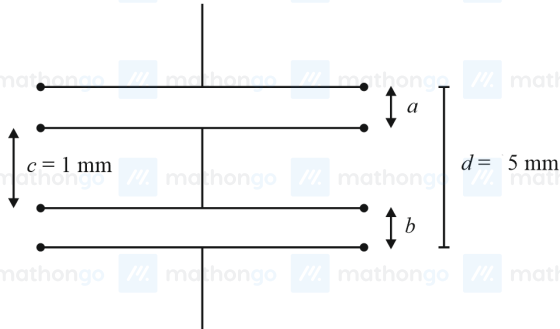2. As shown in the figure, two parallel plate capacitors having equal plate area of 200 cm^2 are joined in such a way that $a \neq b$. The equivalent capacitance of the combination is $x\epsilon_0 F$. The value of x is _____.



[2023 (06 Apr Shift 2)]

3. A 600 pF capacitor is charged by 200 V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. Electrostatic energy lost in the process is _____ μJ .

[2023 (08 Apr Shift 2)]

4. The equivalent capacitance of the combination shown is



[2023 (10 Apr Shift 1)]

- (1) 2 C
(2) $\frac{5}{3} \text{ C}$
(3) $\frac{C}{2}$
(4) 4 C
5. The distance between two plates of a capacitor is d and its capacitance is C_1 , when air is the medium between the plates. If a metal sheet of thickness $\frac{2d}{3}$ and of the same area as plate is introduced between the plates, the capacitance of the capacitor becomes C_2 . The ratio $\frac{C_2}{C_1}$ is

[2023 (10 Apr Shift 2)]

- (1) $3 : 1$
(2) $2 : 1$
(3) $4 : 1$
(4) $1 : 1$

6. The electric field in an electromagnetic wave is given as

$\vec{E} = 20 \sin \omega \left(t - \frac{x}{c} \right) \hat{j} \text{ N C}^{-1}$, where ω and c are angular frequency and velocity of electromagnetic wave respectively. The energy contained in a volume of $5 \times 10^{-4} \text{ m}^3$ will be

(Given $\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2 \text{ N}^{-1} \text{ m}^{-2}$)

[2023 (11 Apr Shift 1)]

- (1) $88.5 \times 10^{-13} \text{ J}$
(2) $17.7 \times 10^{-13} \text{ J}$
(3) $28.5 \times 10^{-13} \text{ J}$
(4) $8.85 \times 10^{-13} \text{ J}$

7. A parallel plate capacitor of capacitance 2 F is charged to a potential V . The energy stored in the capacitor is E_1 . The capacitor is now connected to another uncharged identical capacitor in parallel combination. The energy stored in the combination is E_2 . The ratio $\frac{E_2}{E_1}$ is

[2023 (11 Apr Shift 1)]

- (1) $2 : 1$
(2) $2 : 3$
(3) $1 : 2$
(4) $1 : 4$

8. A capacitor of capacitance C is charged to a potential V . The flux of the electric field through a closed surface enclosing the positive plate of the capacitor is:

[2023 (11 Apr Shift 2)]

- (1) $\frac{CV}{\epsilon_0}$
(2) Zero
(3) $\frac{2CV}{\epsilon_0}$
(4) $\frac{CV}{2\epsilon_0}$

9. In the given circuit. $C_1 = 2\mu\text{F}$, $C_2 = 0.2\mu\text{F}$, $C_3 = 2\mu\text{F}$, $C_4 = 4\mu\text{F}$, $C_5 = 2\mu\text{F}$, $C_6 = 2\mu\text{F}$. The charge stored on capacitor C_4 is μC .



[2023 (11 Apr Shift 2)]

10. In the network shown below, the charge accumulated in the capacitor in steady state will be:



[2023 (13 Apr Shift 2)]


- (1) $10.3\mu\text{C}$
(2) $4.8\mu\text{C}$
(3) $12\mu\text{C}$
(4) $7.2\mu\text{C}$

11. In the circuit shown, the energy stored in the capacitor is $n\mu\text{J}$. The value of n is _____.



[2023 (13 Apr Shift 2)]

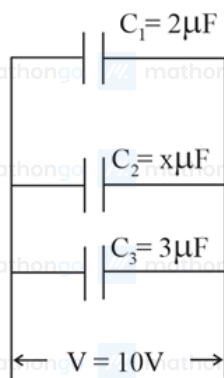12. In the given figure the total charge stored in the combination of capacitors is $100\ \mu\text{C}$. The value of ' x ' is _____.



[2023 (15 Apr Shift 1)]

ANSWER KEYS

1. (3) 2. (5) 3. (6) 4. (1) 5. (1) 6. (4) 7. (3) 8. (1)
9. (4) 10. (4) 11. (75) 12. (5)

1. (3)

The formula to calculate the capacitance of a parallel plate capacitor having thickness d and with a dielectric of thickness x between the plates is given by

$$C = \frac{\epsilon_0 A}{(d-x) + \frac{x}{K}} \dots (1)$$

Substitute the values of the parameters for first case into equation (1) to obtain the capacitance.

$$C_1 = \frac{\epsilon_0 A}{\frac{2d}{3} + \frac{d}{4}} \dots (2)$$

Similarly, substitute the parameters into equation (1) for the second case to obtain the capacitance

$$C_2 = \frac{\epsilon_0 A}{\frac{d}{3} + \frac{2d}{4}} \dots (3)$$

Divide equation (3) by equation (2) to obtain the capacitance in the second case.

$$\frac{C_2}{C_1} = \frac{\frac{2\epsilon_0 A}{d}}{\frac{4\epsilon_0 A}{3d}} = \frac{3}{2}$$

$$C_2 = \frac{3}{2} C_1 \dots (4)$$

Substitute the value of the capacitance in the first case into equation (4) to obtain the value of the capacitance in the second case.

$$C_2 = \frac{3}{2} \times 2 \mu\text{F} = 3 \mu\text{F}$$

2. (5)

The given data is

$$A = 200 \times 10^{-4} \text{ m}^2$$

$$d = 5 \times 10^{-3} \text{ m}$$

$$\text{The value of } a + b = 4 \times 10^{-3} \text{ m}$$

The formula for a parallel plate capacitor is

$$C = \frac{\epsilon_0 A}{D}$$

Let the capacitor with gap a be C_1 and capacitor with gap b be C_2

$$C_1 = \frac{\epsilon_0 A}{a}, C_2 = \frac{\epsilon_0 A}{b}$$

The equivalent capacitance is

$$\frac{1}{C_{eq}} = \frac{a}{\epsilon_0 A} + \frac{b}{\epsilon_0 A}$$

$$\Rightarrow C_{eq} = \frac{\epsilon_0 A}{a+b}$$

It is given that $C_{eq} = x\epsilon_0 \text{ F}$

So,

$$\frac{\epsilon_0 A}{a+b} = x\epsilon_0$$

$$\Rightarrow x = \frac{A}{a+b}$$

$$\Rightarrow x = \frac{200 \times 10^{-4}}{4 \times 10^{-3}} = 5$$

3. (6)

The formula to calculate the initial energy stored in the first capacitor is given by

$$U_i = \frac{1}{2} CV^2 \dots (1)$$

The formula to calculate the final energy stored when two capacitors are connected is given by

$$U_f = \frac{1}{2} C \left(\frac{V}{2} \right)^2 \times 2 \\ = \frac{1}{4} CV^2 \dots (2)$$


Subtract equation (2) from equation (1) to obtain the energy loss (ΔU).

$$\Delta U = \frac{1}{2} CV^2 - \frac{1}{4} CV^2 \\ = \frac{CV^2}{4} \dots (3)$$

Substitute the values of the known parameters into equation (3) to calculate the required loss.

$$\Delta U = \frac{600 \times 10^{-12} \times (200)^2}{4} \text{ J} \\ = 6 \mu\text{J}$$

4. (1)

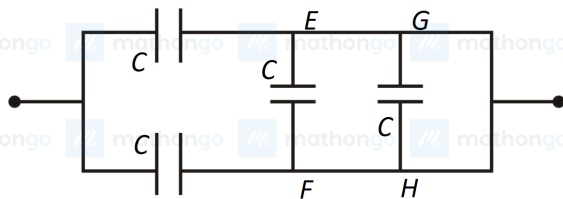


The potential difference across the branches EF & GH is zero. So, the equivalent capacitance will be only due to the combination of two capacitors in parallel.


$$C_{eq} = C + C$$

$$\Rightarrow C_{eq} = 2C$$

5. (1)

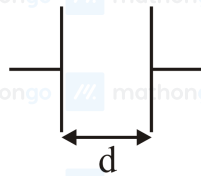

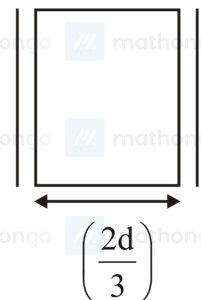The formula of capacitance is $C_1 = \left(\frac{\epsilon_0 A}{d} \right)$



The dielectric constant of metal sheet is $K_{metal} = \infty$

The new value of capacitance is

$$C_2 = \frac{\epsilon_0 A}{d - t + \frac{t}{K_{metal}}} = \frac{\epsilon_0 A}{d - \frac{2d}{3} + 0} = 3C_1$$

Clearly, the ratio,

$$\frac{C_2}{C_1} = \frac{3C_1}{C_1} = 3 : 1$$

6. (4)

Given that, $\vec{E} = 20 \sin \omega \left(t - \frac{x}{c} \right) \hat{j} \text{ N C}^{-1}$

The average energy density of an electromagnetic wave is $\frac{1}{2} \epsilon_0 E_0^2$.

The total energy stored is

$$E_{\text{total}} = \frac{1}{2} \epsilon_0 E_0^2 \times \text{volume}$$

$$\Rightarrow E_{\text{total}} = \frac{1}{2} \times 8.85 \times 10^{-12} \times (20)^2 \times 5 \times 10^{-4}$$


$$= 8.85 \times 10^{-13} \text{ J}$$

7. (3)

The charge on the plates of the first capacitor when connected against the potential difference V is given by

$$Q = CV$$

$$= 2V$$

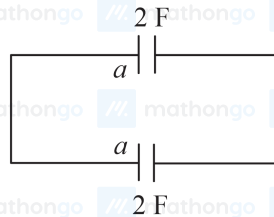

When both the capacitors are connected, from the conservation of charge, it can be written that

$$2V = 2V' + 2V'$$

$$\Rightarrow V' = \left(\frac{1}{2} V \right)$$

where, V' is the new potential difference across each capacitor.

The formula to calculate the energy stored in the first capacitor is given by

$$E_1 = \frac{1}{2} \times C \times V^2$$

$$= \frac{1}{2} \times 2 \times V^2$$

$$= V^2 \dots (1)$$

For the second case, the energy stored in the combination of capacitor is given by

$$E_2 = \frac{1}{2} n CV'^2$$

$$= \frac{1}{2} \times 2 \times \frac{V^2}{4} \times 2$$


$$= \left(\frac{V^2}{2} \right) \dots (2)$$

Divide equation (2) by equation (1) to obtain the required ratio of the stored energy.

$$\frac{E_2}{E_1} = \frac{\frac{V^2}{2}}{V^2}$$

$$= \left(\frac{1}{2} \right)$$

8. (1)

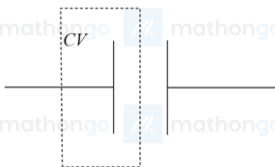

The charge enclosed is given by $q_{\text{enc}} = CV$

Gauss' law states that the flux through any closed surface is equal to the charge enclosed by the surface.

Using Gauss' law the flux is, $\phi = \frac{q_{\text{enc}}}{\epsilon_0} = \left(\frac{CV}{\epsilon_0} \right)$

9. (4)

From the diagram of the circuit, C_3 , C_4 , C_5 are in series, so the total capacitance is

$$\frac{1}{C'} = \frac{1}{2} + \frac{1}{4} + \frac{1}{2}$$

$$\Rightarrow C' = \frac{4}{5} \mu\text{F}$$

C' & C_2 are parallel, the total capacitance is


$$C'' = \left(\frac{4}{5} + 0.2 \right) \mu\text{F} = 1 \mu\text{F}$$

C_1 , C'' , C_6 are in series. So the equivalent capacitance is,

$$\frac{1}{C_{eq}} = \frac{1}{2} + 1 + \frac{1}{2}$$

$$\Rightarrow C_{eq} = 0.5 \mu\text{F}$$

Using $Q = C_{eq}V$.

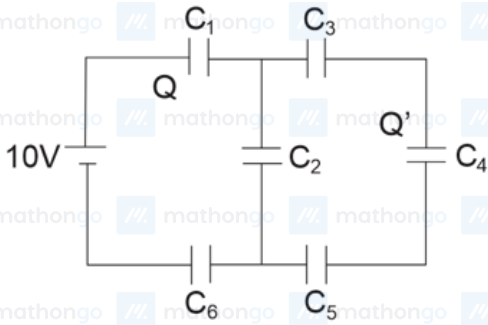

The charge through the battery, $Q = 10 \times \frac{1}{2} = 5 \mu\text{C}$

From the diagram above,

$$Q' = \frac{5 \mu\text{C} \times 0.8}{0.8 + 0.2} = 4 \mu\text{C}$$

10. (4)

In steady state, capacitor behaves as open circuit, so no current will flow.

The total resistance of the circuit is, $R = (6 + 4) \Omega = 10 \Omega$

The current flowing through the circuit is

$$I = \frac{3 \text{ V}}{10 \Omega}$$

Potential difference on 6Ω resistor

$$V' = \frac{3}{10} \times 6 = 1.8 \text{ V}$$

The charge on the capacitor is,

$$Q = CV' = 4 \mu\text{F} \times 1.8 \text{ V} = 7.2 \mu\text{C}$$

11. (75)

The capacitor works as an open circuit in the given configuration.

The potential difference between the two plates of the capacitor will be the difference across the resistors having resistances 3Ω and 4Ω .

Hence, the potential difference (ΔV) across the capacitor can be calculated as follows:

$$\Delta V = \left(\frac{4}{6} \times 12 - \frac{3}{12} \times 12 \right) \text{ V}$$

$$= 5 \text{ V}$$

The formula to calculate the energy stored in the capacitor is given by

$$U = \frac{1}{2} C (\Delta V)^2 \dots (1)$$

Substitute the values of the known parameters into equation (1) to calculate the required energy stored.

$$U = \frac{1}{2} \times 6 \mu\text{F} \times (5 \text{ V})^2$$

$$= 75 \mu\text{J}$$

12. (5) mathongo mathongo mathongo mathongo mathongo mathongo mathongo mathongo mathongo mathongo mathongo

All the capacitors are in parallel combination and therefore potential drop across each capacitor would be the same.

Charge on the capacitor can be written as, $Q = CV$.

The charge on C_1 is $Q_1 = 2 \times 10 = 20 \mu\text{C}$

The charge on C_2 is $Q_2 = x \times 10 = 10x \mu\text{C}$

The charge on C_3 is $Q_3 = 3 \times 10 = 30 \mu\text{C}$

By the given data.

$$C_1 + C_2 + C_3 = 100 \mu\text{C}$$

$$\Rightarrow 10(2 + x + 3) = 100$$

$$\Rightarrow x = 5$$