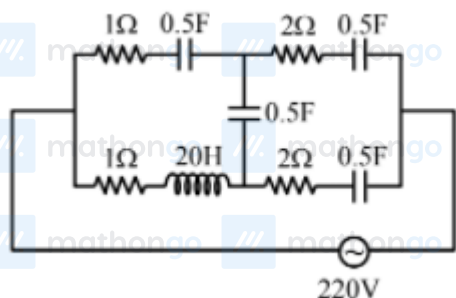


Q1 2021 (31 Aug Shift 2)

At very high frequencies, the effective impedance of the given circuit will be Ω



Q2 2021 (31 Aug Shift 1)

In an ac circuit, an inductor, a capacitor and a resistor are connected in series with $X_L = R = X_C$. Impedance of this circuit is:

- (1) $2R^2$
- (2) Zero
- (3) R
- (4) $R\sqrt{2}$

Q3 2021 (27 Aug Shift 2)

An ac circuit has an inductor and a resistor of resistance R in series, such that $X_L = 3R$. Now, a capacitor is added in series such that $X_C = 2R$. The ratio of new power factor with the old power factor of the circuit is

$\sqrt{5} : x$. The value of x is

Q4 2021 (27 Aug Shift 1)


The alternating current is given by

$$i = \left\{ \sqrt{42} \sin\left(\frac{2\pi}{T}t\right) + 10 \right\} \text{ A}$$

The r.m.s. value of this current is A.

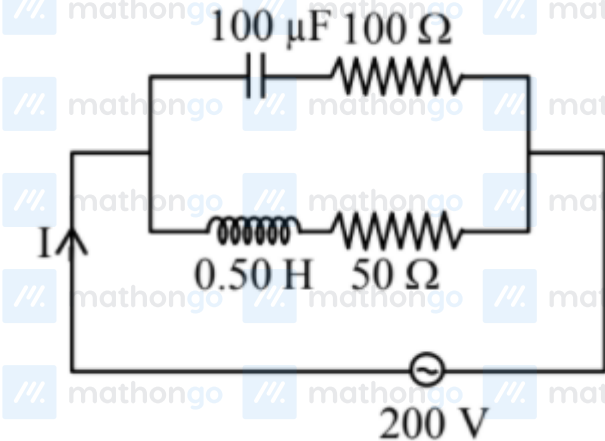Q5 2021 (26 Aug Shift 2)

In the given circuit the AC source has $\omega = 100 \text{ rad s}^{-1}$. Considering the inductor and capacitor to be ideal, what will be the current I flowing through the circuit?



(1) 5.9 A

(2) 4.24 A

(3) 0.94 A

(4) 6 A

Q6 2021 (26 Aug Shift 1)

A series LCR circuit driven by 300 V at a frequency of 50 Hz contains a resistance $R = 3 \text{ k}\Omega$ an inductor of inductive reactance $X_L = 250\pi \Omega$ and an unknown capacitor. The value of capacitance to maximize the average power should be : (Take $\pi^2 = 10$)

(1) $4 \mu\text{F}$

(2) $25 \mu\text{F}$

(3) $400 \mu\text{F}$

(4) $40 \mu\text{F}$

Q7 2021 (26 Aug Shift 1)

An inductor coil stores 64 J of magnetic field energy and dissipates energy at the rate of 640 W when a current of 8 A is passed through it. If this coil is joined across an ideal battery, find the time constant of the circuit in seconds :

- (1) 0.4
- (2) 0.8
- (3) 0.125
- (4) 0.2

Answer Key

Q1 (2)

Q2 (3)

Q3 (1)

Q4 (11)

Q5 (2)

Q6 (1)

Q7 (4)

Q1 (2)

$$X_L = 2\pi fL$$

f is very large


∴ X_L is very large hence open circuit.

$$X_C = \frac{1}{2\pi fC}$$

f is very large.

∴ X_C is very small, hence short circuit.

Final circuit

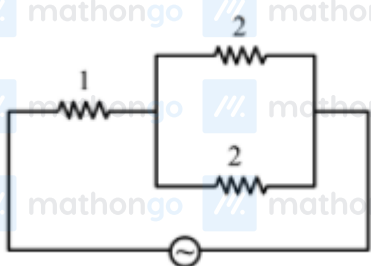


$$Z_{eq} = 1 + \frac{2 \times 2}{2+2} = 2$$

Q2 (3)

$$Z = \sqrt{(X_L - X_C)^2 + R^2} = R \quad \because X_L = X_C$$

Option (3)

Q3 (1)

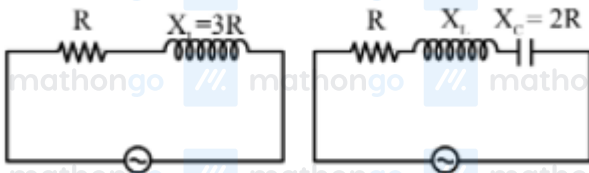

$$\begin{aligned}\cos \phi &= \frac{R}{\sqrt{R^2 + 3R^2}} & \cos \phi' &= \frac{R}{\sqrt{R^2 + R^2}} \\ &= \frac{1}{\sqrt{10}} & &= \frac{1}{\sqrt{2}} \\ \frac{\cos \phi'}{\cos \phi} &= \frac{\frac{1}{\sqrt{2}}}{\frac{1}{\sqrt{10}}} = \frac{\sqrt{10}}{\sqrt{2}} = \frac{\sqrt{5}}{1} \therefore x = 1\end{aligned}$$

Q4 (11)

$$\begin{aligned}f_{\text{rms}}^2 &= f_1^2 + f_2^2 \\ &= \left(\frac{\sqrt{42}}{\sqrt{2}}\right)^2 + 10^2 \\ &= 121 \Rightarrow f_{\text{rms}} = 11 \text{ A}\end{aligned}$$

Q5 (2)

$$\begin{aligned}Z_C &= \sqrt{\left(\frac{1}{\omega C}\right)^2 + R^2} \\ &= \sqrt{\left(\frac{1}{100 \times 100 \times 10^{-6}}\right)^2 + 100^2} \\ Z_c &= \sqrt{(100)^2 + (100)^2}\end{aligned}$$

$$= 100\sqrt{2}$$

$$Z_L = \sqrt{(\omega L)^2 + R^2}$$

$$\sqrt{(100 \times 0.5)^2 + 50^2}$$


$$= 50\sqrt{2}$$

$$i_c = \frac{200}{z_c} = \frac{200}{100\sqrt{2}} = \sqrt{2}$$

$$i_L = \frac{200}{z_L} = \frac{200}{50\sqrt{2}} = 2\sqrt{2}$$

$$\cos \phi_1 = \frac{100}{10\sqrt{2}} = \frac{1}{\sqrt{2}} \Rightarrow \phi_1 = 45^\circ$$
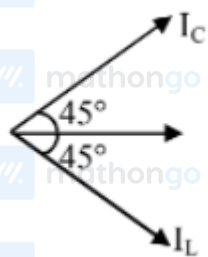
$$\cos \phi_2 = \frac{50}{50\sqrt{2}} = \frac{1}{\sqrt{2}} \Rightarrow \phi_2 = 45^\circ$$



$$\begin{aligned}
 I &= \sqrt{I_C^2 + I_L^2} \\
 &= \sqrt{2 + 8} \\
 &= \sqrt{10} \\
 I &= 3.16 \text{ A}
 \end{aligned}$$

Q6 (1)

For maximum average power

$$X_L = X_C$$

$$250\pi = \frac{1}{2\pi(50)C}$$

$$C = 4 \times 10^{-6}$$

Option (1)

Q7 (4)

$$U = \frac{1}{2}Li^2 = 64 \Rightarrow L = 2$$

$$i^2R = 640R = \frac{640}{(8)^2} = 10$$

$$\tau = \frac{L}{R} = \frac{1}{5} = 0.2$$

Option (4)

#MathBoleTohMathonGo