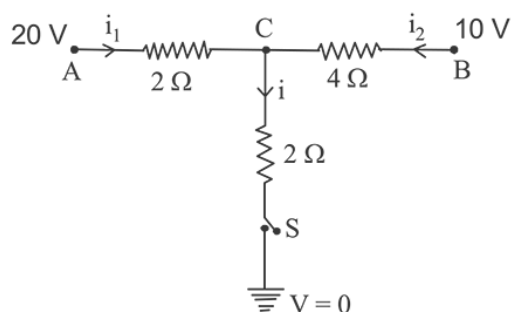


JEE Mains 2019 Chapter wise Question Bank

Current Electricity - Questions

Q1

When the switch S , in the circuit shown, is closed then the value of current i will be:




- (1) 3A (2) 5A
(3) 4A (4) 2A

9 Jan Morning

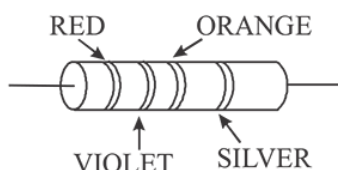Q2

A resistance is shown in the figure. Its value and tolerance are given respectively by:



- (1) $270\ \Omega$, 10% (2) $27\ \text{k}\Omega$, 10%
(3) $27\ \text{k}\Omega$, 20% (4) $270\ \Omega$, 5%

9 Jan Morning

Q3

Drift speed of electrons, when 1.5 A of current flows in a copper wire of cross section $5\ \text{mm}^2$, is v . If the electron density in copper is $9 \times 10^{28}/\text{m}^3$ the value of v in mm/s close to (Take charge of electron to be $= 1.6 \times 10^{-19}\text{C}$)

- (1) 0.02 (2) 3
(3) 2 (4) 0.2

9 Jan Morning

Q4

A carbon resistance has following colour code. What is the value of the resistance?




- (1) $530\ \text{k}\Omega \pm 5\%$ (2) $5.3\ \text{k}\Omega \pm 5\%$
(3) $6.4\ \text{M}\Omega \pm 5\%$ (4) $64\ \text{M}\Omega \pm 10\%$

9 Jan Evening

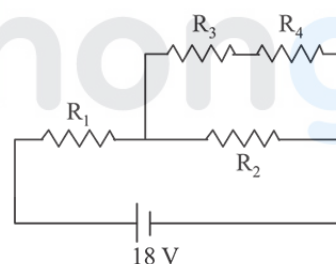Q5

In the given circuit the internal resistance of the 18 V cell is negligible. If $R_1 = 400\ \Omega$, $R_3 = 100\ \Omega$ and $R_4 = 500\ \Omega$ and the reading of an ideal voltmeter across R_4 is 5 V, then the value of R_2 will be:



- (1) $300\ \Omega$ (2) $450\ \Omega$
(3) $550\ \Omega$ (4) $230\ \Omega$

9 Jan Evening

Q6

A uniform metallic wire has a resistance of $18\ \Omega$ and is bent into an equilateral triangle. Then, the resistance between any two vertices of the triangle is:

- (1) $4\ \Omega$ (2) $8\ \Omega$ (3) $12\ \Omega$ (4) $2\ \Omega$

10 Jan Morning

Q7

Current Electricity


A 2 W carbon resistor is color coded with green, black, red and brown respectively. The maximum current which can be passed through this resistor is:

- (1) 20 mA (2) 100 mA
(3) 0.4 mA (4) 63 mA

10 Jan Morning

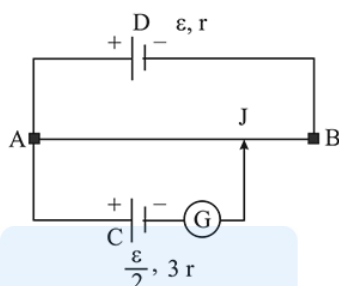Q8

A potentiometer wire AB having length L and resistance $12r$ is joined to a cell D of emf ϵ and internal resistance r . A cell C having emf $\epsilon/2$ and internal resistance $3r$ is connected. The length AJ at which the galvanometer as shown in fig. shows no deflection is:




- (1) $\frac{11}{12}L$ (2) $\frac{11}{24}L$ (3) $\frac{13}{24}L$ (4) $\frac{5}{12}L$

10 Jan Morning

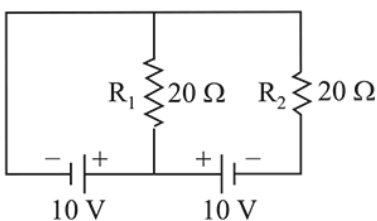Q9

In the given circuit the cells have zero internal resistance. The currents (in Amperes) passing through resistance R_1 and R_2 respectively, are:



- (1) 1, 2 (2) 2, 2
(3) 0.5, 0 (4) 0, 1

10 Jan Morning


Q10

JEE Mains 2019 Chapter wise Question Bank

The actual value of resistance R , shown in the figure is 30Ω . This is measured in an experiment as shown using

the standard formula $R = \frac{V}{I}$, where V and I are the

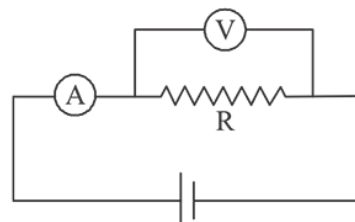reading of the voltmeter and ammeter, respectively. If the measured value of R is 5% less, then the internal resistance of the voltmeter is:



- (1) 600Ω (2) 570Ω
(3) 35Ω (4) 350Ω

10 Jan Evening

Q11

A current of 2 mA was passed through an unknown resistor which dissipated a power of 4.4 W. Dissipated power when an ideal power supply of 11 V is connected across it is:

- (1) $11 \times 10^{-5} \text{ W}$ (2) $11 \times 10^{-3} \text{ W}$
(3) $11 \times 10^{-4} \text{ W}$ (4) $11 \times 10^5 \text{ W}$


10 Jan Evening

Q11

Current Electricity

The Wheatstone bridge shown in Fig. here, gets balanced when the carbon resistor used as R_1 has the colour code (Orange, Red, Brown). The resistors R_2 and R_4 are $80\ \Omega$ and $40\ \Omega$, respectively.

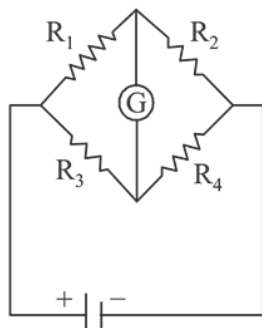Assuming that the colour code for the carbon resistors gives their accurate values, the colour code for the carbon resistor, used as R_3 , would be:




- (1) Brown, Blue, Brown (2) Brown, Blue, Black
(3) Red, Green, Brown (4) Grey, Black, Brown





10 Jan Evening

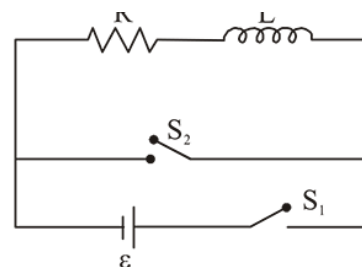Q12

JEE Mains 2019 Chapter wise Question Bank



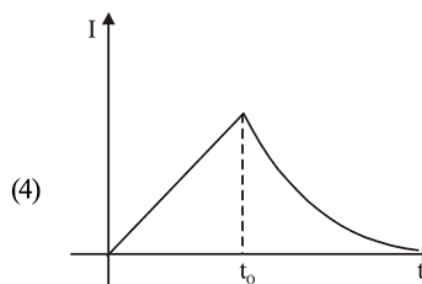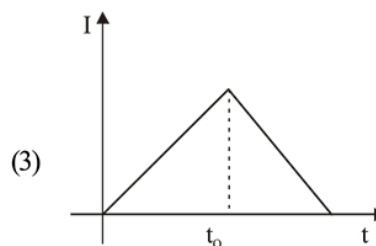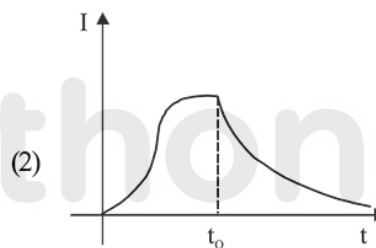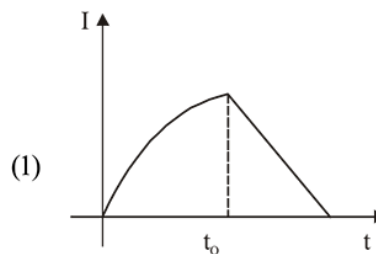the switch S_1 is closed at time $t = 0$ and the switch S_2 is kept open. At some later time (t_0), the switch S_1 is opened and S_2 is closed. the behaviour of the current I as a function of time ' t ' is given by:




11 Jan Morning

Current Electricity

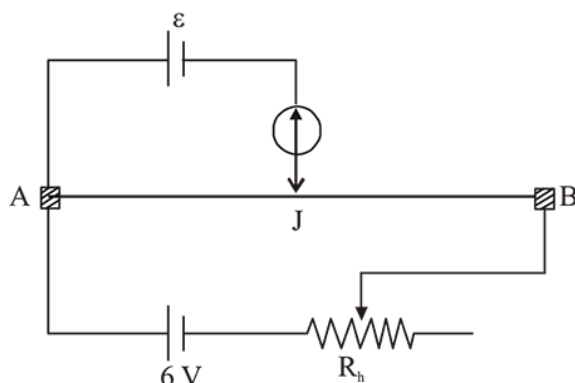Q13

The resistance of the meter bridge AB in given figure is 4Ω . With a cell of emf $\varepsilon = 0.5\text{ V}$ and rheostat resistance $R_h = 2\Omega$ the null point is obtained at some point J. When the cell is replaced by another one of emf $\varepsilon = \varepsilon_2$ the same null point J is found for $R_h = 6\Omega$. The emf ε_2 is:



- | | |
|-----------|-----------|
| (1) 0.4 V | (2) 0.3 V |
| (3) 0.6 V | (4) 0.5 V |

11 Jan Morning

Q14

Two equal resistances when connected in series to a battery, consume electric power of 60 W. If these resistance are now connected in parallel combination to the same battery, the electric power consumed will be :


- | | |
|-----------|-----------|
| (1) 60 W | (2) 240 W |
| (3) 120 W | (4) 30 W |

11 Jan Morning

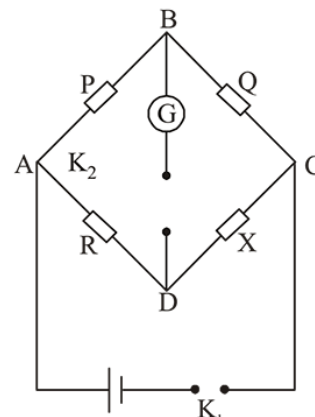Q14

JEE Mains 2019 Chapter wise Question Bank

In a Wheatstone bridge (see fig.), Resistances P and Q are approximately equal. When $R = 400\Omega$, the bridge is balanced. On interchanging P and Q, the value of R, for balance, is 405Ω . The value of X is close to :




- | | |
|---------------|---------------|
| (1) 401.5 ohm | (2) 404.5 ohm |
| (3) 403.5 ohm | (4) 402.5 ohm |

11 Jan Morning

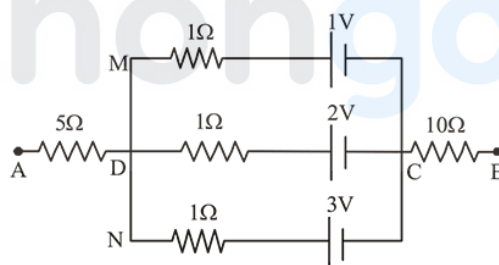Q15

In the circuit shown, the potential difference between A and B is :



- | | |
|---------|---------|
| (1) 1 V | (2) 2 V |
| (3) 3 V | (4) 6 V |

11 Jan Evening

Q16

A galvanometer having a resistance of 20Ω and 30 division on both sides has figure of merit 0.005 ampere/division. The resistance that should be connected in series such that it can be used as a voltmeter upto 15 volt, is:


- | | |
|-----------------|-----------------|
| (1) 100Ω | (2) 120Ω |
| (3) 80Ω | (4) 125Ω |

11 Jan Evening

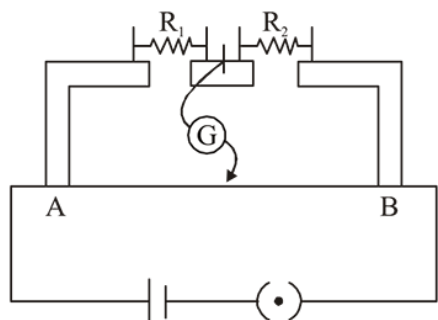Q17

Current Electricity

In the experimental set up of metre bridge shown in the figure, the null point is obtained at a distance of 40 cm from A. If a $10\ \Omega$ resistor is connected in series with R_1 , the null point shifts by 10 cm. The resistance that should be connected in parallel with $(R_1 + 10)\ \Omega$ such that the null point shifts back to its initial position is :



- (1) $20\ \Omega$ (2) $40\ \Omega$
(3) $60\ \Omega$ (4) $30\ \Omega$

11 Jan Evening

Q18

Two electric bulbs, rated at (25 W, 220 V) and (100 W, 220 V), are connected in series across a 220 V voltage source. If the 25 W and 100 W bulbs draw powers P_1 and P_2 respectively, then:

- (1) $P_1 = 16\ \text{W}$, $P_2 = 4\ \text{W}$ (2) $P_1 = 16\ \text{W}$, $P_2 = 9\ \text{W}$
(3) $P_1 = 9\ \text{W}$, $P_2 = 16\ \text{W}$ (4) $P_1 = 4\ \text{W}$, $P_2 = 16\ \text{W}$


1

12 Jan Morning

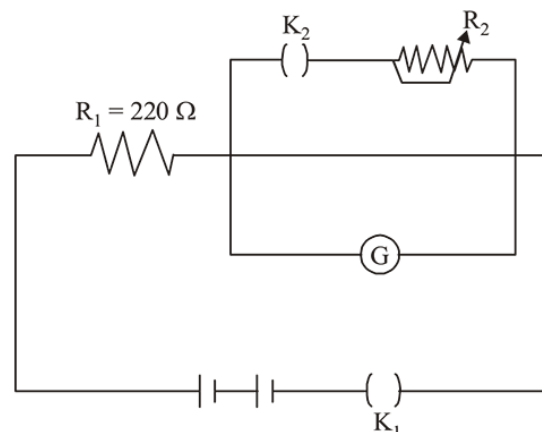Q19

JEE Mains 2019 Chapter wise Question Bank

The galvanometer deflection, when key K_1 is closed but K_2 is open, equals θ_0 (see figure). On closing K_2 also and adjusting R_2 to $5\ \Omega$, the deflection in galvanometer becomes $\frac{\theta_0}{5}$. The resistance of the galvanometer is, then, given by [Neglect the internal resistance of battery]:




- (1) $5\ \Omega$ (2) $22\ \Omega$
(3) $25\ \Omega$ (4) $12\ \Omega$

12 Jan Morning

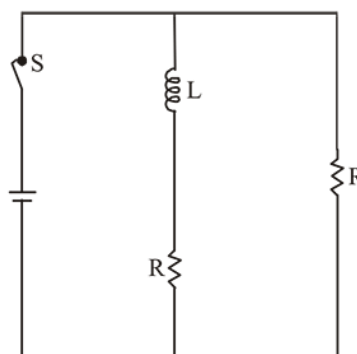Q20

In the figure shown, a circuit contains two identical resistors with resistance $R = 5\ \Omega$ and an inductance with $L = 2\ \text{mH}$. An ideal battery of 15 V is connected in the circuit. What will be the current through the battery long after the switch is closed?



- (1) 5.5 A (2) 7.5 A
(3) 3 A (4) 6 A


12 Jan Morning

Q21

Current Electricity

In a meter bridge, the wire of length 1 m has a non-uniform cross-section such that, the variation $\frac{dR}{dl}$ of its resistance

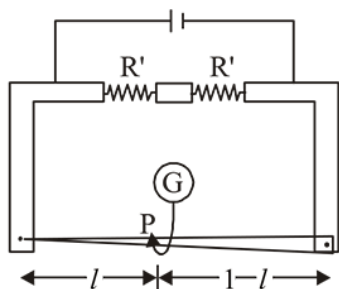R with length l is $\frac{dR}{dl} \propto \frac{1}{\sqrt{l}}$. Two equal resistances are connected as shown in the figure. The galvanometer has zero deflection when the jockey is at point P. What is the length AP?



- (1) 0.2m (2) 0.3m
(3) 0.25m (4) 0.35m

12 Jan Morning

Q22


An ideal battery of 4 V and resistance R are connected in series in the primary circuit of a potentiometer of length 1 m and resistance 5Ω . The value of R , to give a potential difference of 5 mV across 10 cm of potentiometer wire is:

- (1) 490Ω (2) 480Ω
(3) 395Ω (4) 495Ω

12 Jan Morning

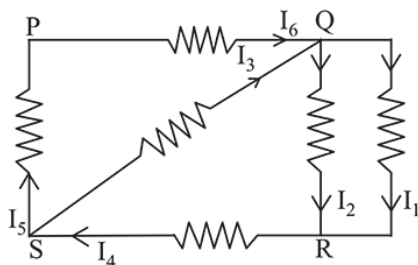Q23

In the given circuit diagram, the currents, $I_1 = -0.3$ A, $I_4 = 0.8$ A and $I_5 = 0.4$ A, are flowing as shown. The currents I_2 , I_3 and I_6 , respectively, are :



- (1) 1.1 A, -0.4 A, 0.4 A (2) 1.1 A, 0.4 A, 0.4 A
(3) 0.4 A, 1.1 A, 0.4 A (4) -0.4 A, 0.4 A, 1.1 A

12 Jan Evening

JEE Mains 2019 Chapter wise Question Bank

Q24


A galvanometer, whose resistance is 50 ohm, has 25 divisions in it. When a current of 4×10^{-4} A passes through it, its needle (pointer) deflects by one division. To use this galvanometer as a voltmeter of range 2.5 V, it should be connected to a resistance of :

- (1) 250 ohm (2) 200 ohm
(3) 6200 ohm (4) 6250 ohm

12 Jan Evening

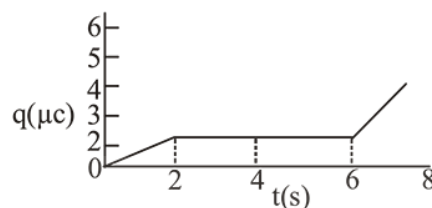Q25

The charge on a capacitor plate in a circuit, as a function of time, is shown in the figure:



What is the value of current at $t = 4$ s ?

- (1) Zero (2) $3 \mu\text{A}$
(3) $2 \mu\text{A}$ (4) $1.5 \mu\text{A}$

12 Jan Evening

Q26


A 200Ω resistor has a certain color code. If one replaces the red color by green in the code, the new resistance will be :

- (1) 100Ω (2) 400Ω (3) 300Ω (4) 500Ω

8 April Morning

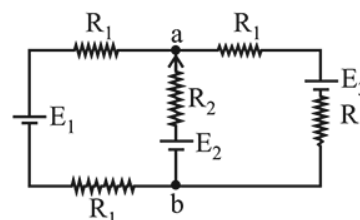Q27

For the circuit shown, with $R_1 = 1.0 \Omega$, $R_2 = 2.0 \Omega$, $E_1 = 2$ V and $E_2 = E_3 = 4$ V, the potential difference between the points 'a' and 'b' is approximately (in V) :




- (1) 2.7 (2) 2.3 (3) 3.7 (4) 3.3

8 April Morning

Current Electricity

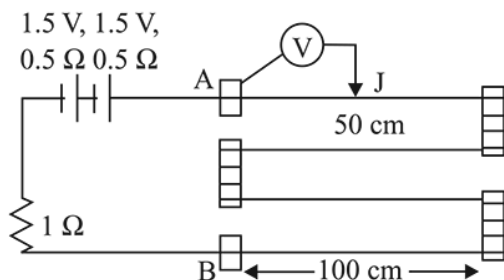Q28

In the circuit shown, a four-wire potentiometer is made of a 400 cm long wire, which extends between A and B. The resistance per unit length of the potentiometer wire is $r = 0.01 \Omega/\text{cm}$. If an ideal voltmeter is connected as shown with jockey J at 50 cm from end A, the expected reading of the voltmeter will be :



- (1) 0.50 V (2) 0.75 V (3) 0.25 V (4) 0.20 V

8 April Evening

Q29

A cell of internal resistance r drives current through an external resistance R . The power delivered by the cell to the external resistance will be maximum when :


- (1) $R = 0.001 r$ (2) $R = 1000 r$
(3) $R = 2r$ (4) $R = r$

8 April Evening

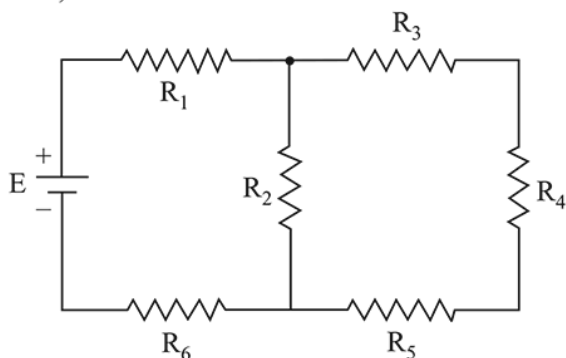Q30

In the figure shown, what is the current (in Ampere) drawn from the battery? You are given :

$R_1 = 15 \Omega$, $R_2 = 10 \Omega$, $R_3 = 20 \Omega$, $R_4 = 5 \Omega$, $R_5 = 25 \Omega$, $R_6 = 30 \Omega$, $E = 15 \text{ V}$




- (1) 13/24 (2) 7/18 (3) 9/32 (4) 20/3

8 April Evening

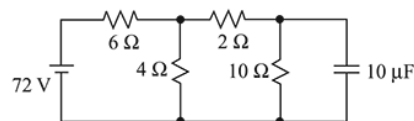Q31

JEE Mains 2019 Chapter wise Question Bank

Determine the charge on the capacitor in the following circuit:




- (1) $60 \mu\text{C}$ (2) $2 \mu\text{C}$
(3) $10 \mu\text{C}$ (4) $200 \mu\text{C}$

9 April Morning

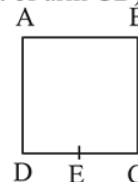Q32

A wire of resistance R is bent to form a square ABCD as shown in the figure. The effective resistance between E and C is: (E is mid-point of arm CD)



- (1) R (2) $\frac{7}{64}R$ (3) $\frac{3}{4}R$ (4) $\frac{1}{16}R$

9 April Morning

Q33

A moving coil galvanometer has resistance 50Ω and it indicates full deflection at 4 mA current. A voltmeter is made using this galvanometer and a $5 \text{ k} \Omega$ resistance. The maximum voltage, that can be measured using this voltmeter, will be close to:

- (1) 40 V (2) 15 V (3) 20 V (4) 10 V

9 April Morning

Q34

A metal wire of resistance 3Ω is elongated to make a uniform wire of double its previous length. This new wire is now bent and the ends joined to make a circle. If two points on the circle make an angle 60° at the centre, the equivalent resistance between these two points will be:

- (1) $\frac{12}{5} \Omega$ (2) $\frac{5}{2} \Omega$ (3) $\frac{5}{3} \Omega$ (4) $\frac{7}{2} \Omega$

9 April Evening

Q35

Current Electricity

The resistance of a galvanometer is 50 ohm and the maximum current which can be passed through it is 0.002 A. What resistance must be connected to it order to convert it into an ammeter of range 0 – 0.5 A?

- (1) 0.5 ohm (2) 0.002 ohm
(3) 0.02 ohm (4) 0.2 ohm

9 April Evening

Q36


In a conductor, if the number of conduction electrons per unit volume is $8.5 \times 10^{28} \text{ m}^{-3}$ and mean free time is 25 fs (femto second), it's approximate resistivity is: ($m_e = 9.1 \times 10^{-31} \text{ kg}$)

- (1) $10^{-6} \Omega\text{m}$ (2) $10^{-7} \Omega\text{m}$ (3) $10^{-8} \Omega\text{m}$ (4) $10^{-5} \Omega\text{m}$

9 April Evening

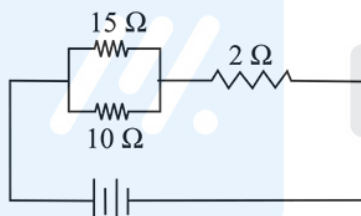Q37

In the given circuit, an ideal voltmeter connected across the 10Ω resistance reads 2V. The internal resistance r , of each cell is :




- (1) 1 Ω (2) 0.5 Ω (3) 1.5 Ω (4) 0 Ω

10 April Morning

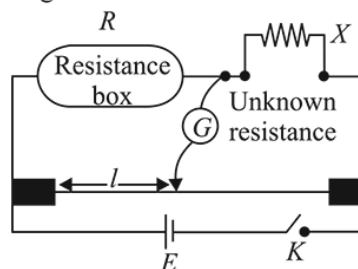Q38

JEE Mains 2019 Chapter wise Question Bank

In a meter bridge experiment, the circuit diagram and the corresponding observation table are shown in figure.



Sl.No.	R	l (cm)
1.	1000	60
2.	100	13
3.	10	1.5
4.	1	1.0

Which of the reading is consistent ?

- (1) 3 (2) 2 (3) 4 (4) 1

10 April Morning

Q39

A current of 5 A passes through a copper conductor (resistivity) = $1.7 \times 10^{-8} \Omega\text{m}$ of radius of cross-section 5 mm. Find the mobility of the charges if their drift velocity is $1.1 \times 10^{-3} \text{ m/s}$.

- (1) $1.8 \text{ m}^2/\text{Vs}$ (2) $1.5 \text{ m}^2/\text{Vs}$
(3) $1.3 \text{ m}^2/\text{Vs}$ (4) $1.0 \text{ m}^2/\text{Vs}$

10 April Morning

Q40

Space between two concentric conducting spheres of radii a and b ($b > a$) is filled with a medium of resistivity p . The resistance between the two spheres will be :


- (1) $\frac{p}{4\pi} \left(\frac{1}{a} - \frac{1}{b} \right)$ (2) $\frac{p}{2\pi} \left(\frac{1}{a} - \frac{1}{b} \right)$
(3) $\frac{p}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$ (4) $\frac{p}{4\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$

10 April Evening

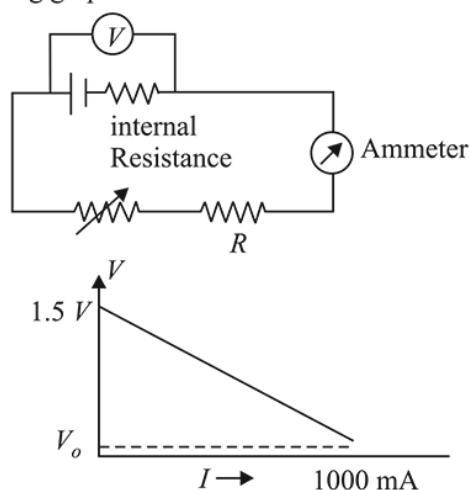Q41

Current Electricity

To verify Ohm's law, a student connects the voltmeter across the battery as, shown in the figure. The measured voltage is plotted as a function of the current, and the following graph is obtained :



If V_o is almost zero, identify the correct statement:

- (1) The emf of the battery is 1.5 V and its internal resistance is 1.5 Ω
- (2) The value of the resistance R is 1.5 Ω
- (3) The potential difference across the battery is 1.5 V when it sends a current of 1000 mA
- (4) The emf of the battery is 1.5 V and the value of R is 1.5 Ω

12 April Morning

Q42

A galvanometer of resistance 100 Ω has 50 divisions on its scale and has sensitivity of 20 $\mu\text{A}/\text{division}$. It is to be converted to a voltmeter with three ranges, of 0–2V, 0–10 V and 0–20 V. The appropriate circuit to do so is :


- (1) $R_1 = 2000 \Omega$
 $R_2 = 8000 \Omega$
 $R_3 = 10000 \Omega$
- (2) $R_1 = 1900 \Omega$
 $R_2 = 9900 \Omega$
 $R_3 = 19900 \Omega$
- (3) $R_1 = 1900 \Omega$
 $R_2 = 8000 \Omega$
 $R_3 = 10000 \Omega$
- (4) $R_1 = 19900 \Omega$
 $R_2 = 9900 \Omega$
 $R_3 = 1900 \Omega$

12 April Morning

JEE Mains 2019 Chapter wise Question Bank

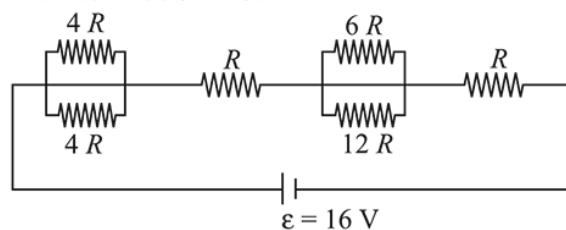Q43

The resistive network shown below is connected to a D.C. source of 16 V. The power consumed by the network is 4 Watt. The value of R is :



- (1) 6 Ω (2) 8 Ω (3) 1 Ω (4) 16 Ω

12 April Morning

Q44

A moving coil galvanometer, having a resistance G, produces full scale deflection when a current I_g flows through it. This galvanometer can be converted into (i) an ammeter of range 0 to I_0 ($I_0 > I_g$) by connecting a shunt resistance R_A to it and (ii) into a voltmeter of range 0 to V ($V = GI_0$) by connecting a series resistance R_V to it. Then,


- (1) $R_A R_V = G^2 \left(\frac{I_0 - I_g}{I_g} \right)$ and $\frac{R_A}{R_V} = \left(\frac{I_g}{I_0 - I_g} \right)^2$
- (2) $R_A R_V = G^2$ and $\frac{R_A}{R_V} = \left(\frac{I_g}{I_0 - I_g} \right)^2$
- (3) $R_A R_V = G^2 \left(\frac{I_g}{I_0 - I_g} \right)$ and $\frac{R_A}{R_V} = \left(\frac{I_0 - I_g}{I_g} \right)^2$
- (4) $R_A R_V = G^2$ and $\frac{R_A}{R_V} = \frac{I_g}{(I_0 - I_g)}$

12 April Evening

JEE Mains 2019 Chapter wise Question Bank

Current Electricity - Answers

Q1

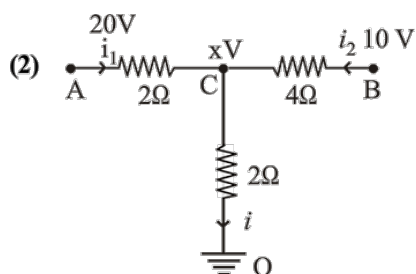

Let voltage at C = xV

From kirchhoff's current law,

KCL : $i_1 + i_2 = i$

$$\frac{20-x}{2} + \frac{10-x}{4} = \frac{x-0}{2} \Rightarrow x = 10$$

$$\therefore i = \frac{V}{R} = \frac{x}{2} = \frac{10}{2} = 5A$$

9 Jan Morning

Q2

(2) Color code: Bl, Br, R, O, Y, G, B, V, Gr, W

0, 1, 2, 3, 4, 5, 6, 7, 8, 9

 $R = AB \times C \pm D\%$ where D = tolerance $D_{\text{gold}} = \pm 5\%$, $D_{\text{silver}} = \pm 10\%$; $D_{\text{no colour}} = \pm 20\%$

Red violet orange silver

$$R = 27 \times 10^3 \Omega \pm 10\%$$

$$i = 27 \text{ k}\Omega \pm 10\%$$

9 Jan Morning

Q3

(1) Using, $I = neAv_d$

$$\therefore \text{Drift speed } v_d = \frac{1}{neA}$$

$$= \frac{1.5}{9 \times 10^{28} \times 1.6 \times 10^{-19} \times 5 \times 10^{-6}} = 0.02 \text{ mm/s}^{-1}$$

9 Jan Morning

Q4

(1) Colour code for carbon resistor

Bl, Br, R, O, Y, G, Blue, V, Gr, W

0 1 2 3 4 5 6 7 8 9

Resistance, $R = AB \times C \pm D$

Bands A and B are the first two significant figures of resistance

B and C indicates the decimal multiplier or the number of zeros that follow A and B


B and D is tolerance: Gold = $\pm 5\%$,Silver = $\pm 10\%$ No colour = $\pm 20\%$

$$R = 53 \times 10^4 \pm 5\% = 530 \text{ k}\Omega \pm 5\%$$

9 Jan Evening

Q5

Current Electricity

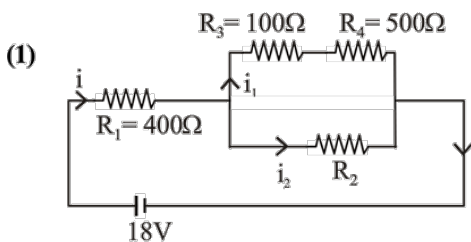

Across R_4 reading of voltmeter, $V_4 = 5V$

$$\text{Current, } i_4 = \frac{V_4}{R_4} = 0.01A$$

$$V_3 = i_1 R_3 = 1V$$

$$V_3 + V_4 = 6V = V_2$$

$$V_1 + V_3 + V_4 = 18V$$

$$\Rightarrow V_1 = 12V$$

$$i = \frac{V_1}{R_1} = 0.03A$$


$$i = i_1 + i_2 \Rightarrow i_2 = i - i_1 = 0.03 - 0.01A = 0.02A$$

$$\therefore R_2 = \frac{V_2}{i_2} = \frac{6}{0.02} = 300\Omega$$

9 Jan Evening

Q6

(1)

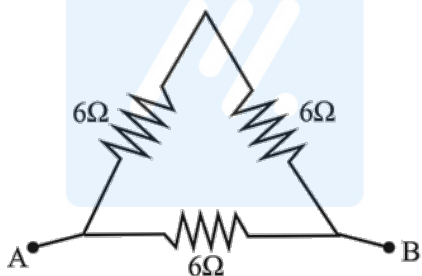

Resistance, $R \propto l$ so resistance of each side of the equilateral triangle = 6Ω

Resistance R_{eq} between any two vertices

$$\frac{1}{R_{eq}} = \frac{1}{12} + \frac{1}{6} \Rightarrow R_{eq} = 4\Omega$$

10 Jan Morning

Q7

JEE Mains 2019 Chapter wise Question Bank

(1) Colour code for carbon resistor

Bl, Br, R, O, Y, G, Blue, V, Gr, W

0 1 2 3 4 5 6 7 8 9

Resistance, $R = AB \times C \pm D$

$\therefore$ Resistance, $R = 50 \times 10^2 \Omega$

Now using formula, Power, $P = i^2 R$

$$\therefore i = \sqrt{\frac{P}{R}} = \sqrt{\frac{2}{50 \times 10^2}} = 20mA$$

10 Jan Morning

Q8

(3) Let x be the length AJ at which galvanometer shows null deflection current,

$$i = \frac{\epsilon}{12r + r} = \frac{3}{13r}$$

$$\text{or, } i \left(\frac{x}{L} 12r \right) = \frac{\epsilon}{2}$$

$$\Rightarrow \frac{\epsilon}{13r} \left[\frac{x}{L} 12r \right] = \frac{\epsilon}{2}$$

$$\text{or, } x = \frac{13L}{24}$$

10 Jan Morning

Q9

(3) Current passing through resistance R_1 ,

$$i_1 = \frac{V}{R_1} = \frac{10}{20} = 0.5A \text{ and, } i_2 = 0$$

10 Jan Morning

Q10

(2) using, $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$

$$0.95 R = \frac{RR_0}{R + R_0} \text{ (measured value 5\% less)}$$

then internal resistance of voltmeter)

$$\text{or, } 0.95 \times 30 = 0.05 R_0$$

$$\therefore R_0 = 19 \times 30 = 570 \Omega$$

10 Jan Evening

Current Electricity

Q11

(1) Power, $P = I^2 R$

$$4.4 = 4 \times 10^{-6} \times R$$

$$\Rightarrow R = 1.1 \times 10^6 \Omega$$

When supply of 11 v is connected

$$\text{Power, } P' = \frac{V^2}{R} = \frac{11^2}{1.1} \times \frac{11^2}{1.1} \times 10^{-6}$$

$$= 11 \times 10^{-5} \text{ W}$$

10 Jan Evening

Q11

(1) Given, colour code of resistance,

R_1 = Orange, Red and Brown

$$\therefore R_1 = 32 \times 10 = 320$$

using balanced wheatstone bridge principle,


$$\frac{R_1}{R_3} = \frac{R}{R_4} \Rightarrow \frac{320}{R_3} = \frac{80}{40}$$

$\therefore R_3 = 160$ i.e. colour code for R_3 Brown, Blue and Brown

10 Jan Evening

Q12

(2)

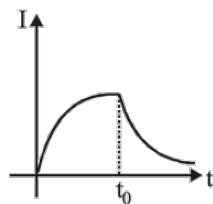

The current will grow for the time $t = 0$ to $t = t_0$ and after that decay of current takes place.

11 Jan Morning

Q13

JEE Mains 2019 Chapter wise Question Bank

(2) Given, Emf of cell, $\varepsilon = 0.5 \text{ v}$

Rheostat resistance, $R_h = 2 \Omega$

Potential gradient is

$$\frac{dv}{dL} = \left(\frac{6}{2+4} \right) \times \frac{4}{L}$$

Let null point be at ℓ cm when cell of emf $\varepsilon = 0.5 \text{ v}$ is used.

$$\text{thus } \varepsilon_1 = 0.5 \text{ V} = \left(\frac{6}{2+4} \right) \times \frac{4}{L} \times \ell \quad \dots (i)$$

For resistance $R_h = 6 \Omega$ new potential gradient is

$$\left(\frac{6}{4+6} \right) \times \frac{4}{L} \text{ and at null point}$$

$$\left(\frac{6}{4+6} \right) \left(\frac{4}{L} \right) \times \ell = \varepsilon_2 \quad \dots (ii)$$

Dividing equation (i) by (ii) we get

$$\frac{0.5}{\varepsilon_2} = \frac{10}{6} \text{ thus } \varepsilon_2 = 0.3$$

11 Jan Morning

Q14

(2) When two resistances are connected in series,

$$R_{eq} = 2R$$

$$\text{Power consumed, } P = \frac{\varepsilon^2}{R_{eq}} = \frac{\varepsilon^2}{2R}$$

In parallel condition, $R_{eq} = R/2$.

$$\text{New power, } P' = \frac{\varepsilon^2}{(R/2)}$$

$$\text{or } P' = 4P = 240 \text{ W } (\because P = 60 \text{ W})$$

11 Jan Morning

Q14

(4)

11 Jan Morning

Q15

Current Electricity

- (2) Given, $E_1 = 1\text{V}$, $E_2 = 2\text{V}$, $E_3 = 3\text{V}$, $r_1 = 1\Omega$,
 $r_2 = 1\Omega$ and $r_3 = 1\Omega$

$$V_{AB} = V_{CD} = \frac{\frac{E_1}{r_1} + \frac{E_2}{r_2} + \frac{E_3}{r_3}}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3}} = \frac{\frac{1}{1} + \frac{2}{1} + \frac{3}{1}}{\frac{1}{1} + \frac{1}{1} + \frac{1}{1}}$$

$$= \frac{6}{3} = 2\text{V}$$

11 Jan Evening

Q16

- (3) Deflection current

$$= I_{g_{\max}} = n \times k = 0.005 \times 30$$

Where, n = Number of divisions = 30 and $k = 0.005$
 amp/division

$$= 15 \times 10^{-2} = 0.15$$

$$v = I_g [20 + R]$$

$$15 = 0.15 [20 + R]$$

$$100 = 20 + R$$

$$R = 80 \Omega$$

11 Jan Evening

Q17

JEE Mains 2019 Chapter wise Question Bank

- (3) Initially at null deflection $\frac{R_1}{R_2} = \frac{2}{3} \dots(i)$

Finally at null deflection, when null point is shifted

$$\frac{R_1 + 10}{R_2} = 1 \Rightarrow R_1 + 10 = R_2 \dots(ii)$$

Solving equations (i) and (ii) we get

$$\frac{2R_2}{3} + 10 = R_2$$

$$10 = \frac{R_2}{3} \Rightarrow R_2 = 30\Omega$$

$$\& R_1 = 20\Omega$$

Now if required resistance is R then

$$\frac{30 \times R}{30 + R} = \frac{2}{3}$$

$$R = 60\Omega$$

11 Jan Evening

Q18

- (1) As $R = \frac{V^2}{P}$, so $R_1 = \frac{220^2}{25}$ and $R_2 = \frac{220^2}{100}$

$$\text{Current flown } i = \frac{220}{R_1 + R_2}$$

$$P_1 = i^2 R_1 = \frac{220^2}{\left(\frac{220^2}{25} + \frac{220^2}{100}\right)} \times \frac{220^2}{25} = 16 \text{ W}$$

$$\text{Similarly, } P_2 = i^2 R_2 = 4 \text{ W}$$

12 Jan Morning

Q19

Current Electricity

- (2) When key K_1 is closed and key K_2 is open

$$i_g = \frac{E}{220 + R_g} = C\theta_0 \quad \dots (i)$$

When both the keys are closed

$$i_g = \left(\frac{E}{220 + \frac{5R_g}{5 + R_g}} \right) \times \frac{5}{(R_g + 5)} = \frac{C\theta_0}{5}$$

$$\Rightarrow \frac{5E}{225R_g + 1100} = \frac{C\theta_0}{5} \quad \dots (ii)$$

$$\frac{E}{220 + R_g} = C\theta_0 \quad \dots (i)$$

Dividing (i) by (ii), we get

$$\Rightarrow \frac{225R_g + 1100}{1100 + 5R_g} = 5$$

$$\Rightarrow 5500 + 25R_g = 225R_g + 1100$$

$$200R_g = 4400$$

$$R_g = 22\Omega$$

12 Jan Morning

Q20

- (4) Long time after switch is closed, the inductor will be idle so, the equivalent diagram will be as below



$$I = \frac{\varepsilon}{\left(\frac{R \times R}{R + R} \right)} = \frac{2\varepsilon}{R} = \frac{2 \times 15}{5} = 6A$$

12 Jan Morning

Q21

JEE Mains 2019 Chapter wise Question Bank

- (3) We have given

$$\frac{dR}{d\ell} \propto \frac{1}{\sqrt{\ell}} \Rightarrow \frac{dR}{d\ell} = k \times \frac{1}{\sqrt{\ell}} \quad (\text{where } k \text{ is constant})$$

$$dR = k \frac{d\ell}{\sqrt{\ell}}$$

Let R_1 and R_2 be the resistance of AP and PB respectively.

Using wheatstone bridge principle

$$\therefore \frac{R_1}{R_2} = \frac{R_1}{R_2} \text{ or } R_1 = R_2$$

$$\text{Now, } \int dR = k \int \frac{d\ell}{\sqrt{\ell}}$$

$$\therefore R_1 = k \int_0^{\ell} \ell^{-1/2} d\ell = k \cdot 2\sqrt{\ell}$$

$$R_2 = k \int_{\ell}^1 \ell^{-1/2} d\ell = k \cdot (2 - 2\sqrt{\ell})$$

Putting $R_1 = R_2$

$$k2\sqrt{\ell} = k(2 - 2\sqrt{\ell})$$

$$\therefore 2\sqrt{\ell} = 1$$


$$\sqrt{\ell} = \frac{1}{2}$$

$$\text{i.e., } \ell = \frac{1}{4} \text{ m} \Rightarrow 0.25 \text{ m}$$

12 Jan Morning

Q22

Current Electricity

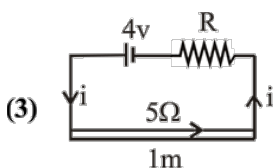

Current flowing through the circuit (I) is given by

$$I = \left(\frac{4}{R+5} \right) A$$

Resistance of length 10 cm of wire

$$= 5 \times \frac{10}{100} = 0.5 \Omega$$

According to question,


$$5 \times 10^{-3} = \left(\frac{4}{R+5} \right) (0.5)$$

$$\therefore \frac{4}{R+5} = 10^{-2} \text{ or } R+5 = 400 \Omega$$

$$\therefore R = 395 \Omega$$

12 Jan Morning

Q23

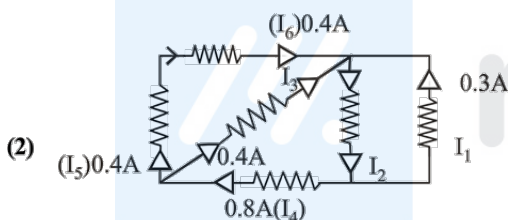

From KCL, $I_3 = 0.8 - 0.4 = 0.4 A$

$$I_2 = 0.4 + 0.4 + 0.3$$


$$= 1.1 A$$

$$\text{and } I_6 = 0.4 A$$

12 Jan Evening

Q24

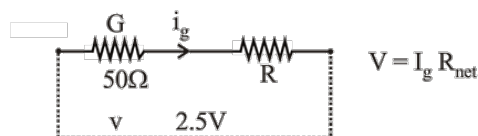(2) Galvanometer has 25 divisions $I_g = 4 \times 10^{-4} \times 25 = 10^{-2} A$



$$v = I_g (G + R)$$

$$2.5 = (50 + R) 10^{-2} \therefore R = 200 \Omega$$

12 Jan Evening

JEE Mains 2019 Chapter wise Question Bank

Q25

(1) Clearly, from graph

$$\text{Current, } I = \frac{dq}{dt} = 0 \text{ at } t = 4s \text{ [Since } q \text{ is constant]}$$

12 Jan Evening

Q26

(4) Number 2 is associated with the red colour. This colour is replaced by green.

$\therefore$ Colour code figure for green is 5

$\therefore$ New resistance = 500 Ω

8 April Morning


Q27

(4) Applying parallel combination of batteries

Equivalent emf between A and B is

$$\frac{E_1}{\frac{1}{1+1}} + \frac{E_2}{\frac{1}{2}} + \frac{E_3}{\frac{1}{1+1}}$$
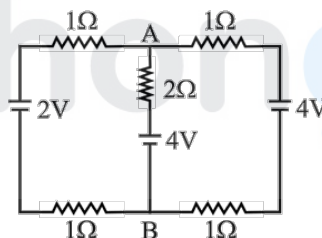
$$= \frac{1+1}{1+1} + \frac{2}{2} + \frac{1+1}{1+1}$$



$$\frac{2}{\frac{1}{2} + \frac{1}{2} + \frac{1}{2}} = \frac{5 \times 2}{3}$$

$$= \frac{10}{3} = 3.3 \text{ Volt}$$

8 April Morning

Q28

(3) The resistance of potentiometer wire

$$R = 0.01 \times 400 = 4 \Omega$$

Current in the wire

$$i = \frac{V}{R_T} = \frac{3}{4 + 0.5 + 0.57 + 1} = \frac{1}{2} A$$

$$\text{Now } V = i R_{AJ} = \frac{1}{2} \times (0.01 \times 50) = 0.25 V.$$

8 April Evening


Current Electricity

Q29

$$(4) i = \left(\frac{\epsilon}{R+r} \right)$$

Power delivered to R.
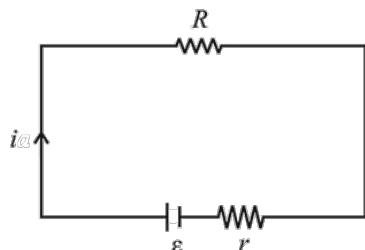
$$P = i^2 R = \left(\frac{\epsilon}{R+r} \right)^2 R$$



P to be maximum, $\frac{dP}{dR} = 0$


$$\text{or } \frac{d}{dR} \left[\left(\frac{\epsilon}{R+r} \right)^2 R \right] = 0$$

$$\text{or } R = r$$

8 April Evening

Q30

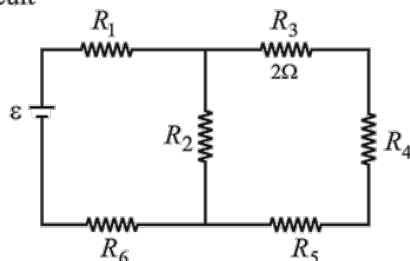- (3) R_3, R_4 and R_5 are in series so their equivalent $R = 20 + 5 + 25 = 50 \Omega$
This is parallel with R_2 , and so net resistance of the circuit



$$R_{eq} = \left(\frac{10 \times 50}{10 + 50} \right) + 15 + 30 = \frac{160}{3} \Omega$$

$$\text{So, } i = \frac{\epsilon}{R_{eq}} = \frac{15}{(100/3)} = \frac{9}{32} A$$

8 April Evening


Q31

JEE Mains 2019 Chapter wise Question Bank

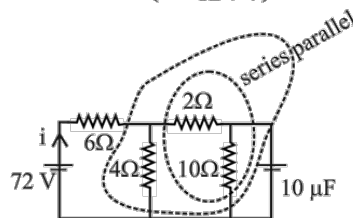- (4) At steady state, there is no current in capacitor.

2Ω and 10Ω are in series. Their equivalent resistance is 12Ω . This 12Ω is in parallel with 4Ω and their combined resistance is $12 \times 4 / (12 + 4)$. This resistance is in series with 6Ω . Therefore, current drawn from battery

$$i = \frac{V}{R} = \left(\frac{72}{6 + \frac{12 \times 4}{12 + 4}} \right) = 8 A$$



Current in 10Ω resistor

$$i' = \left(\frac{4}{4 + 12} \right) 8 = 2 A$$

Pd across capacitor, $V = i' R = 2 \times 10 = 20V$

$\therefore$ Charge on the capacitor, $q = CV$

$$= 10 \times 20 = 200 \mu C.$$


9 April Morning

Q32

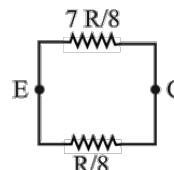- (2) Here $R_{DA} = R_{AB} = R_{BC} = R/4$
and $R_{DE} = R_{EC} = R/8$
Now $R_{ED}, R_{DA}, R_{AB}, R_{BC}$ are in series.

$$\therefore R_s = \frac{R}{8} + \frac{R}{4} + \frac{R}{4} + \frac{R}{4} = \frac{R + 2R + 2R + 2R}{8} = \frac{7R}{8}$$

$$\therefore R_{eq} = \frac{\left(\frac{7R}{8} \right) \left(\frac{R}{8} \right)}{R} = \frac{7R}{64}$$



9 April Morning

Q33

- (3) $V = i_g (G + R) = 4 \times 10^{-3}$
 $(50 + 5000) = 20V$

9 April Morning


Q34

Current Electricity

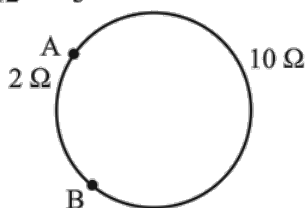- (3) When length becomes double its resistance becomes
 $(R \propto l^2)$

$$R = 4 \times 3 = 12 \Omega$$

$$R_{eq} = \frac{2 \times 10}{12} = \frac{5}{3} \Omega$$



9 April Evening

Q35

(4) Using, $i_g = i \frac{S}{S+G}$

$$0.002 = 0.5 \frac{S}{S+50}$$

On solving, we get

$$S = \frac{100}{498} \approx 0.2 \Omega$$

9 April Evening

Q36

(3) $\rho = \frac{m}{ne^2\tau}$

$$= \frac{9.1 \times 10^{-31}}{8.5 \times 10^{28} \times (1.6 \times 10^{-19})^2 \times 25 \times 10^{-15}}$$


$$= 10^{-8} \Omega\text{-m}$$

9 April Evening

Q37

JEE Mains 2019 Chapter wise Question Bank

- (2) For the given circuit

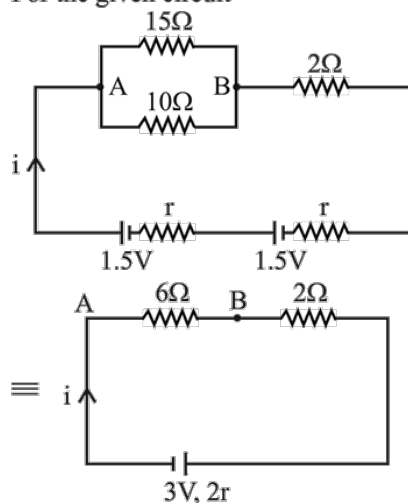

$$i = \frac{3}{8+2r}$$

Now voltage across AB

$$i \times 6 = \frac{3}{8+2r} \times 6 = 2$$

$$\Rightarrow 9 = 8 + 2r$$

$$\Rightarrow r = \frac{1}{2} \Omega$$

10 April Morning

Q38

- (3) For a balanced bridge

$$\frac{R_1}{R_2} = \frac{l_2}{l_1}$$

$$\text{So } \frac{R}{X} = \frac{l}{100-l}$$

Using the above expression

$$X = \frac{R(100-l)}{l}$$

$$\text{for observation (1) } X = \frac{100 \times 40}{60} = \frac{2000}{3} \Omega$$

$$\text{for observation (2) } X = \frac{100 \times 87}{13} = \frac{8700}{13} \Omega$$

$$\text{for observation (3) } X = \frac{10 \times 98.5}{1.5} = \frac{1970}{3} \Omega$$

$$\text{for observation (4) } X = \frac{1 \times 99}{1} = 99 \Omega$$

Clearly we can see that the value of x calculated in observation (4) is inconsistent than other.

10 April Morning

Q39

Current Electricity

(4) Charge mobility

$$(\mu) = \frac{V_d}{E} \quad [\text{Where } V_d = \text{drift velocity}]$$

$$\text{and resistivity } (\rho) = \frac{E}{j} = \frac{EA}{I} \Rightarrow E = \frac{I(\rho)}{A}$$

$$\Rightarrow \mu = \frac{V_d}{E} = \frac{V_d A}{I \rho}$$

$$= \frac{1.1 \times 10^{-3} \times \pi \times (5 \times 10^{-3})^2}{5 \times 1.7 \times 10^{-8}}$$

$$\mu = 1.0 \frac{\text{m}^2}{\text{Vs}}$$

10 April Morning

Q40


$$(1) dR = \frac{(\rho)(dx)}{4\pi x^2}$$

$$R = \int dR$$

$$\int dR = \rho \int_a^b \frac{dx}{4\pi x^2}$$

$$\Rightarrow R = \frac{\rho}{4\pi} \left[\frac{-1}{x} \right]_a^b$$
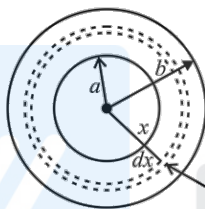
$$R = \left(\frac{\rho}{4\pi} \right) \cdot \left(\frac{1}{a} - \frac{1}{b} \right)$$



10 April Evening

Q41

$$(1) \text{ When } i = 0, V = \varepsilon = 1.5 \text{ volt}$$

12 April Morning

Q42

$$(3) i_g = 20 \times 50 = 1000 \mu\text{A} = 1 \text{ mA}$$

Using, $V = i_g (G + R)$, we have

$$2 = 10^{-3} (100 + R_1)$$

$$R_1 = 1900 \Omega$$

when, $V = 10 \text{ volt}$

$$10 = 10^{-3} (100 + R_2 + R_1)$$

$$10000 = (100 + R_2 + 1900)$$

$$\therefore R_2 = 8000 \Omega$$

12 April Morning

Q43

JEE Mains 2019 Chapter wise Question Bank

(2) Equivalent resistance,

$$R_{eq} = \frac{4R \times 4R}{4R + 4R} + R + \frac{6R \times 12R}{6R + 12R} + R$$

$$= 2R + R + 4R + R$$

$$= 8R.$$

$$\text{Using, } P = \frac{V^2}{R_{eq}}$$

$$4 = \frac{16^2}{8R}$$

$$\therefore R = \frac{16^2}{4 \times 8} = 8 \Omega$$

12 April Morning

Q44

(2) In an ammeter,

$$i_g = i_0 \frac{R_A}{R_A + G}$$

and for voltmeter,

$$V = i_g (G + R_v) = G i_0$$

On solving above equations, we get

$$R_A R_v = G^2$$

$$\text{and } \frac{R_A}{R_v} = \left(\frac{i_g}{i_0 - i_g} \right)^2$$

12 April Evening